



Sem IV ET CBQS A/E 2

1915113

QP Code : NP-19691

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question No. 1 is Compulsory.
(2) Solve any three questions from remaining five questions.
(3) Figures to the right indicate full marks.
(4) Assume suitable data if necessary and mention the same in answer sheet.

1. Solve any five

20

- Compare ideal and practical Op Amp.
- Consider a BJT has parameters $f_T = 500$ MHz at $I_C = 1$ mA, $\beta = 100$ and $C_\mu = 0.3$ pF. Calculate bandwidth f_p and capacitance C_π of a BJT.
- What is cross-over distortion in power Amplifier. How it is overcome?
- Which type of biasing technique is used to bias Integrated Circuit and why?
- Find output voltage of differential amplifier if its differential gain $A_d = 100$, common mode gain $A_c = 0.1$ and input voltage are $V_1 = 2 + 0.55 \sin \omega t$ and $V_2 = 0.5 - 0.005 \sin \omega t$.
- Explain line regulation and load regulation of voltage regulator. Draw load and line regulation characteristics of ideal and practical voltage regulator.

2. (a) For the circuit shown in Fig 2a, the parameters are $R_s = 0.1$ k Ω , $R_1 = 20$ k Ω , $R_2 = 2.2$ k Ω , $R_e = 0.1$ K Ω , $C_c = 47$ μ f, and $V_{CC} = 10$ V. The transistor parameters are : $V_{BE(ON)} = 0.7$ V, $\beta = 200$, and $V_A = \infty$. 10
- Derive expression for lower cut-off frequency (or time constant) due to coupling capacitor C_c ,
 - Determine lower cut off frequency and midband voltage gain.

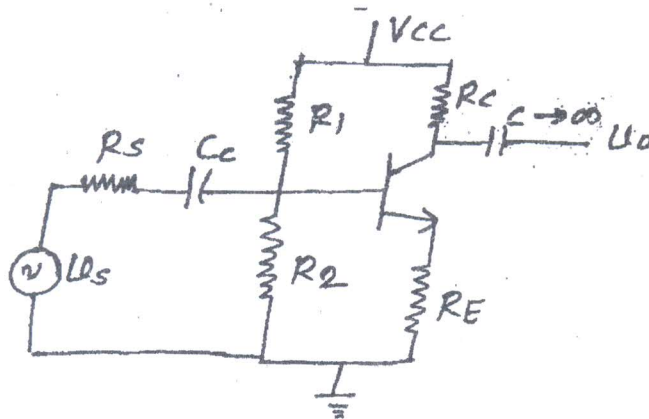


Fig 2a

Con. 10712-14.

[TURN OVER



2. (b) For the circuit shown Fig.2b, the transistor parameters are : $K_n = 1\text{mA/V}^2$, $V_{TN} = 0.8\text{V}$, $\lambda = 0$, $C_{gs} = 2\text{pF}$, and $c_{gd} = 0.2\text{pF}$. Determine
- (i) Miller capacitance
 - (ii) The upper 3dB (high cut-off) frequency
 - (iii) The mid band voltage gain

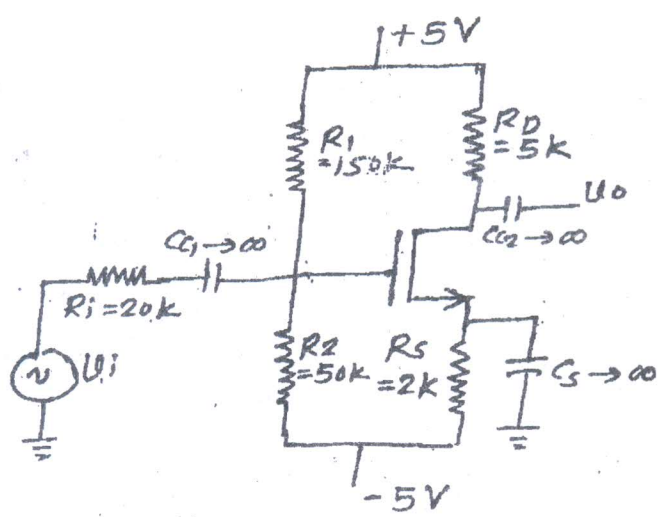


Fig. 2b

3. (a) For the circuit shown in Fig.3a, find overall midband voltage gain and capacitors C_{c1} and C_{c2} such that the 3dB frequencies associated with each stage are equal. Assume BJT have parameters : $V_{BE(ON)} = 0.7\text{V}$, $\beta = 200$, and $V_A = \infty$.

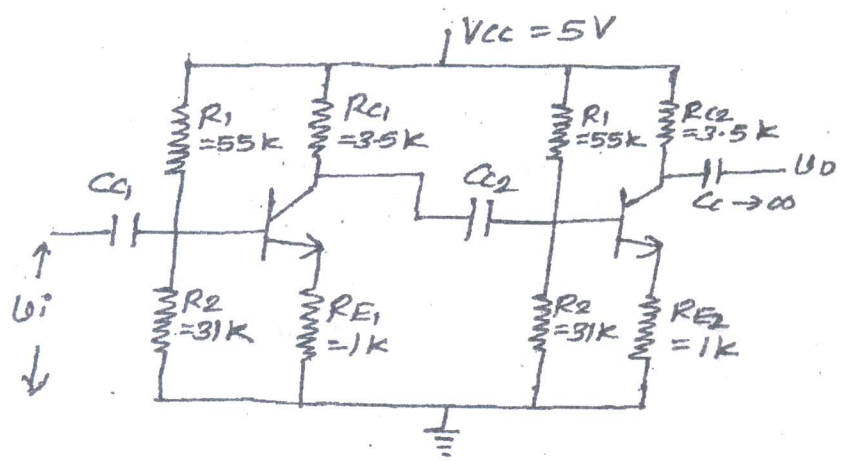


Fig. 3a



3. (b) For the differential amplifier shown in Fig 3b, derive expression for differential voltage gain, common-mode voltage gain and CMRR. 10

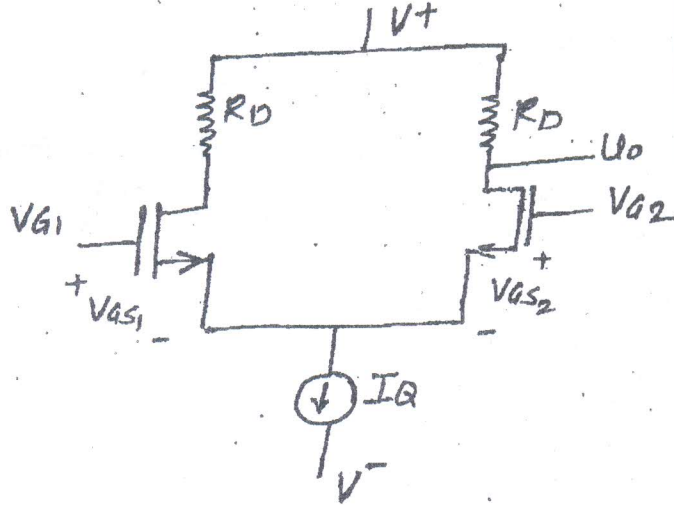


Fig 3b

4. (a) The transistor parameters for the circuit shown in Fig 4a are $\beta = 100$, $V_{BE(ON)} = 0.7V$, and $V_A = \infty$. 10
- (i) Determine R_E such that $I_E = 150 \mu A$.
 - (ii) Find A_d , A_{cm} and CMRR for one sided output at U_{02} .
 - (iii) Determine the differential and common-mode input resistances.

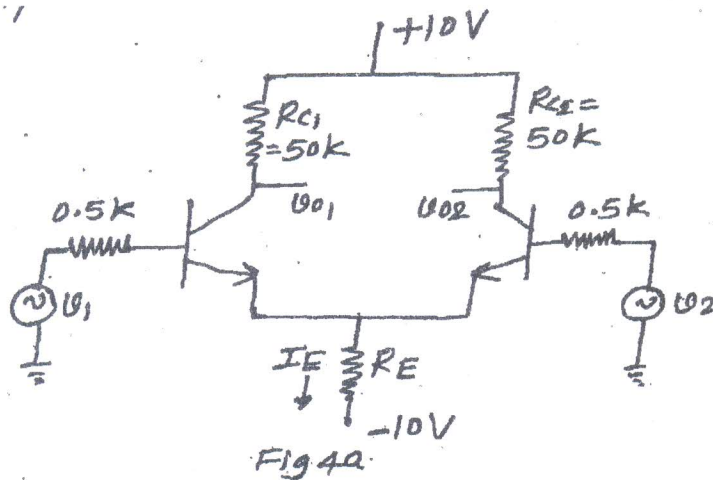


Fig 4a

