



QP Code : NP-19679

(3 hours)


[Total Marks : 80

- N.B.: (1) Question no. 1 is compulsory.
 (2) Solve any three out of remaining questions.
 (3) Assume suitable data wherever necessary.

1. Solve any four :-

20

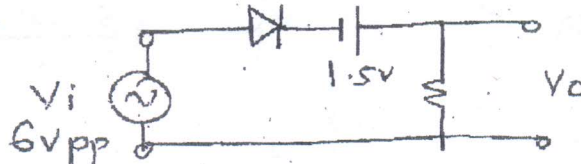
- (a) For the following clipper circuit sketch the i/p and o/p wave form write equation for V_o . 5



- (b) Compare BJT, JFET and MOSFET. 5
 (c) Which components in an amplifier (CS and CE) circuit affect low frequency response? Explain. 5
 (d) State and explain Barkhausen's criteria. 5
 (e) Explain effect of swamping resistor in differential amplifier. 5
 (f) Derive expression of efficiency of class A Transformer coupled amplifier. 5

2. (a) Draw approximate hybrid π model of CE transistor amplifier and derive expressions for A_v , A_i , Z_i and Z_o . 10

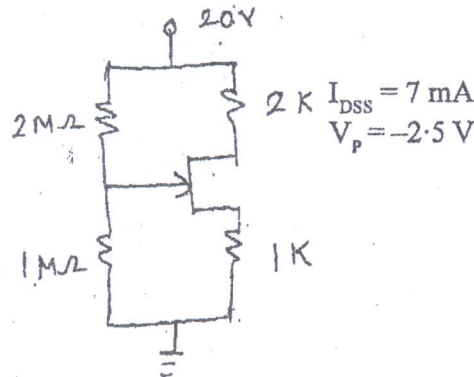- (b) Determine operating point and draw DC load line for the circuit shown :- 10




3. (a) Draw two stage CS-CS amplifier circuit and derive expressions for A_v , Z_i and Z_o . 10
 (b) State different types of negative feedback topologies and explain current series in detail using block diagram. 10

4. (a) Draw circuit diagram for dual i/p balanced o/p differential amplifier (using any type of devices) and derive expressions for A_d , A_c , CMRR and R_i . 10

- (b) Draw circuit diagram of colpitt's oscillator and explain it's working. State applications, advantages and disadvantages of this circuit. 10


[TURN OVER

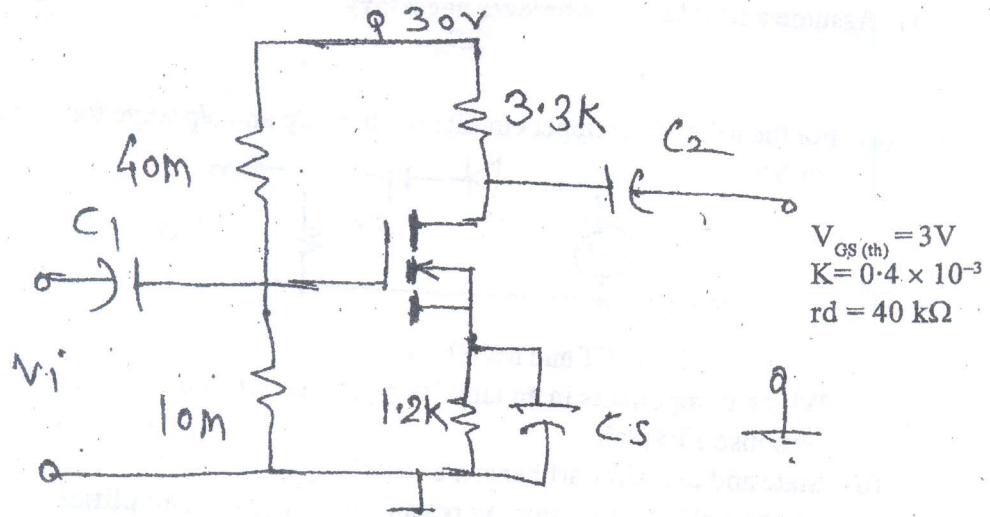5. (a) Justify need for constant current source and explain any one in detail. 10
 (b) Explain working of class B (push-pull) power amplifier. 10
6. (a) For the circuit shown find A_v , R_i and R_o . 10



- (b) Draw High frequency model for CS JFET amplifier and explain. 5
 (c) Explain importance and need for biasing in amplifier. 5

Con. 12016-14.

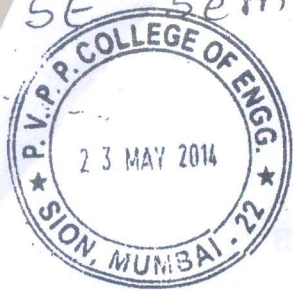

SE Sem IV Elex, EXTC (CBAS)

AM - IV

23/05/2014

QP Code : NP-19713

(3 Hours)

[Total Marks : 80

- N.B.: (1) Questions No. 1 is compulsory.
(2) Solve any three from the remaining.

1. (a) Prove that Eigen values of a hermitian matrix are real. 5

(b) Evaluate $\oint_C \frac{e^{kz}}{z} dz$ over the circle $|z|=1$ and k is real. Hence prove 5

that $\int_0^\pi e^{k \cos \theta} \cos(k \sin \theta) d\theta = 2\pi$.

(c) Find the extremal of $\int_{x_2}^{x_1} (16y^2 - (y'')^2 + x^2) dx$ 5

(d) Find a vector orthogonal to both $u = (-6, 4, 2)$ and $v = (3, 1, 5)$. 5

2. (a) Find the curve $y = f(x)$ for which $\int_{x_1}^{x_2} y\sqrt{1+(y')^2} dx$ is minimum subject to the 6

constraint $\int_{x_1}^{x_2} \sqrt{1+(y')^2} dx = \ell$.

(b) Find eigen values and eigen vectors of the matrix $A = \begin{bmatrix} -2 & 5 & 4 \\ 5 & 7 & 5 \\ 4 & 5 & -2 \end{bmatrix}$ 6

(c) Obtain Taylor's series and two distinct Laurent's series expansion of 8

$f(z) = \frac{z^2 - 1}{z^2 + 5z + 6}$ about $z=0$, indicating region of convergence.

3. (a) State Cayley-Hamilton Theroern, hence deduce that $A^8 = 625I$, where 6

$A = \begin{bmatrix} 1 & 2 \\ 2 & -1 \end{bmatrix}$

(b) Using calculus of Residues, prove that $\int_0^{2\pi} e^{\cos \theta} \cos(\sin \theta - n\theta) d\theta = \frac{2\pi}{n!}$. 6

(c) Find the plane curve of fixed perimeter and maximum area. 8

[TURN OVER

Con. 11555-14.



4. (a) State Cauchy-Schwartz inequality and hence show that 6

$$\left(x^2 + y^2 + z^2\right)^{1/2} \geq \frac{1}{13} (3x + 4y + 12z), \quad x, y, z \text{ are positive.}$$

- (b) Reduce the quadratic form $Q = x^2 + y^2 - 2z^2 - 4xy - 2yz + 10xz$ to Canonical form using congruent transformation. 6

- (c) (i) If $A = \begin{bmatrix} \pi/2 & 3\pi/2 \\ \pi & \pi \end{bmatrix}$, find $\sin A$. 4

- (ii) Show that the matrix $A = \begin{bmatrix} 5 & -6 & -6 \\ -1 & 4 & 2 \\ 3 & -6 & -4 \end{bmatrix}$ is Derogatory. 4

5. (a) Using Rayleigh - Ritz method, find an appropriate solution for the extremal of the 6

$$\text{functional } I[y(x)] = \int_0^1 \left[xy + \frac{1}{2}(y')^2 \right] dx \text{ subject to } y(0) = y(1) = 0.$$

- (b) Find an orthonormal basis of the following subspace of \mathbb{R}^3 , $S = \{ [1, 2, 0] [0, 3, 1] \}$. 6

- (c) Is the matrix $A = \begin{bmatrix} 2 & 1 & 1 \\ 1 & 2 & 1 \\ 0 & 0 & 1 \end{bmatrix}$ diagonalizable. If so find diagonal form and transforming matrix. 8

6. (a) Find $f(3)$, $f'(1+i)$, $f''(1-i)$, if $f(a) = \oint_c \frac{3z^2 + 11z + 7}{z-a} dz$, $c: |z|=2$. 6

- (b) Evaluate $\int_0^\infty \frac{x^3 \sin x}{(x^2 + a^2)^2} dx$ using contour integration. 6

- (c) Find the singular value decomposition of the matrix $A = \begin{bmatrix} 1 & 1 \\ 1 & 1 \\ 1 & -1 \end{bmatrix}$. 8

M.P.P.
(3 Hours)

QP Code : NP-19758

[Total Marks : 80

- N.B. : 1. Question no. 1 is compulsory
2. Solve any three from the remaining five questions.
3. Assume suitable additional data if necessary.

Q1) Answer the following questions: (20 marks)

- Explain flag register of 8085 microprocessor.
- What is REP prefix? How it functions for string instructions?
- Explain the feature of pipelining and queue in 8086 architecture.
- Explain the significance of HOLD, RESET and READY signals in 8086 processor.
- For 8086 op-code fetch machine cycle explain the significance of each T-state.

Q2)a) Draw and explain the instruction template format of 8086 processor ?

(10marks)

b) Explain programmable interrupt controller 8259 – features and operation.

(10 marks)

Q3) a) Explain 8086-8087 coprocessor configuration in maximum mode of operation. (10 marks)

b) Explain the following 8086 instructions

a) CMPSB b) DIV AX c) LOOPE again d) REP SCASB e) XLATB

(10marks)

Q4) a) Write a detailed note on the interrupt structure of 8086 processor. (6 marks)

b) What are the basic modes of operation of 8255, Explain with the format of control register. (4marks)

b) Explain the need for DMA and modes of DMA data transfer.

(10 marks)

Q5) a) Explain the architecture of 8086 processor. What is the need for memory segmentation. (10 marks)

b) With the help of a neat flowchart/algorithm write a program in 8086 assembly to arrange a set of ten 8-bit numbers initialized in data segment in ascending order. (10 marks)

Q6) a) Write a brief note on programmable peripheral interface (PPI) IC – 8255 and its modes of operation. (10 marks)

b) Using string instructions write a program in 8086 assembly to copy a block ten bytes initialized in data segment to extra segment. Assume the necessary details. (10 marks)

Con. 12200-14.





PCS

QP Code : NP-19794

(3 Hours)


[Total Marks : 80

- N.B. (1) Question No. 1 is compulsory.
 (2) Attempt any three questions from remaining questions.
 (3) Assume suitable data wherever necessary.

1. Attempt any four :-


20

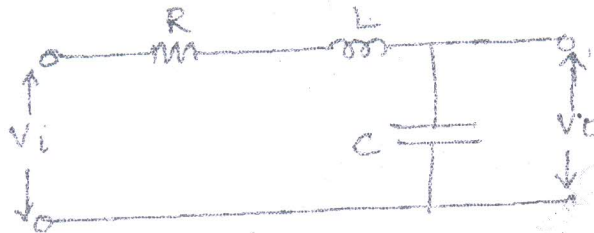- (a) Differentiate between feedback and feed forward control system.
 (b) What is a compensator? Why is it required?
 (c) What are the properties of state transition matrix?
 (d) Explain the concept of absolute, relative and robust stability.
 (e) Find the transfer function for following network.



2. (a) Obtain the transfer function of the mechanical system.

10

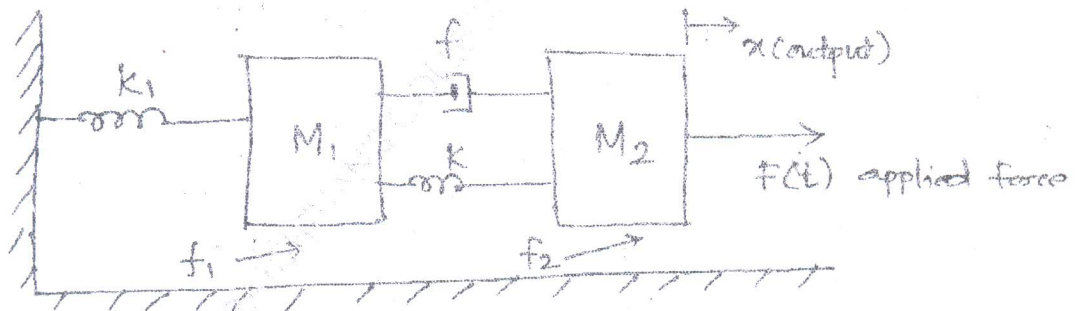

(b) Consider unity feedback control system with an open loop transfer function of -

10

$$G(s) = \frac{k(s+1)(s+2)}{(s+0.1)(s-1)}$$

- (i) Plot the root loci showing asymptotes, centroid, break away point, the gain at which root locus crosses $j\omega$ axis.
 (ii) Find value of gain for which a closed system is critically damped.

Con. 13032-14.

[TURN OVER



3. (a) A unity feedback control system is characterized by the open loop transfer function. 10

$$G(s) = \frac{k(s+13)}{s(s+3)(s+7)}$$

using the Routh criterion, calculate the range of values of k for system to be stable.

- (b) Write a note on advances in control systems. 10

4. (a) Obtain the state variable model of the transfer function- 10

$$\frac{Y(s)}{U(s)} = \frac{s^2 + 3s + 3}{s^2 + 2s + 3s + 1}$$

- (b) Sketch the Bode plot for the open loop transfer function given by- 10

$$G(s)H(s) = \frac{0.5(1+5s)}{s^2(1+0.5s)}$$

5. (a) Find rise time, settling time and peak overshoot for the system given by transfer function-

$$G(s) = \frac{25}{(s^2 + 8s + 25)}$$

- (b) Using Nyquist criterion, determine the closed loop system having following open loop transfer function is stable or not. If not, find number of poles in right half of s plane - 5


$$G(s)H(s) = \frac{1+4s}{s^2(1+s)(1+2s)}$$

- (c) Check controllability and observability for the system- 10

$$\dot{x} = \begin{bmatrix} 1 & 2 & 1 \\ 0 & 1 & 3 \\ 1 & 1 & 1 \end{bmatrix} x + \begin{bmatrix} 1 \\ 0 \\ 2 \end{bmatrix} u$$

$$y = [1 \ 3 \ 0] x$$

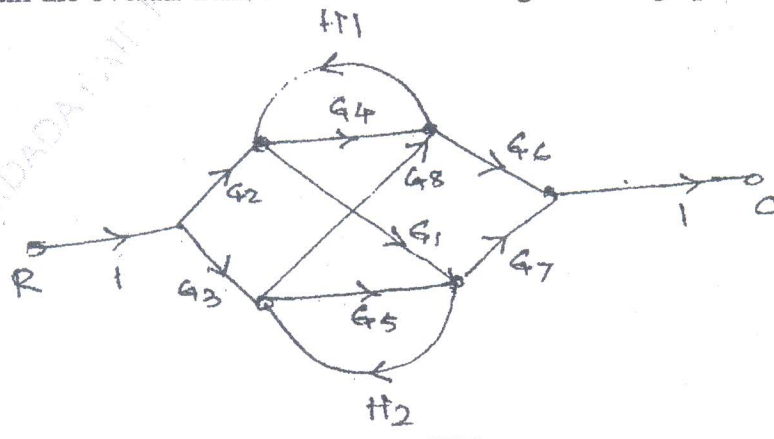6. (a) Explain the concept of on-off controller using example. 5
 (b) Compare lead-lag compensator. 5
 (c) Obtain the overall transfer function from signal flow graph. 10





Sem IV Eley old Maths

(OLD COURSE)

QP Code : MV-18801

(3 Hours)

[Total Marks : 100

- N. B. : (1) Question No. 1 is compulsory.
(2) Attempt any four questions from the remaining six questions.
(3) Figures to the right indicate full marks.

1. (a) The probability distribution of a random variable X is given by 5
$$\begin{array}{cccccc} X & : & -2 & -1 & 0 & 1 & 2 & 3 \\ P(X=x) & : & 0.1 & K & 0.2 & 2K & 0.3 & K \end{array}$$

Find K, mean and variance.
- (b) Find the eigen values and eigen vectors of the matrix $\begin{bmatrix} 2 & -1 & 1 \\ 1 & 2 & -1 \\ 1 & -1 & 2 \end{bmatrix}$ 5
- (c) Find the residue at the pole for $\frac{ze^z}{(z-a)^3}$ 5
- (d) Let R be the relation defined on Z by $x R y$ if $|x-y|$ is divisible by 5. Show that R is an equivalence relation. 5
2. (a) Evaluate $\int_c \frac{3z^2 + z}{z^2 - 1} dz$ where c is $|z| = 2$ 6
- (b) Can it be concluded that the average life-span of an Indian is more than 70 years, if a random sample of 100 Indian has an average life-span of 71.8 years with standard deviation of 7.8 years. 6
- (c) Show that the matrix A is diagonalisable. Find the transforming matrix and the diagonal matrix where $A = \begin{bmatrix} 8 & -8 & -2 \\ 4 & -3 & -2 \\ 3 & -4 & 1 \end{bmatrix}$ 8
3. (a) Find the mean and variance of the poisson distribution 6
- (b) Find A^n if $A = \begin{bmatrix} 7 & 3 \\ 2 & 6 \end{bmatrix}$ 6
- (c) Evaluate $\int_0^{2\pi} \frac{d\theta}{3 + 2\cos\theta}$ 8



4. (a) A manufacturer knows from his experience that the resistance of resistors he produces is normal with $\mu=100$ ohms and $\sigma = 2$ ohms. What percentage of resistors will have resistance between 98 ohms and 102 ohms? 6
- (b) If $f(x)=2x+5$, $g(x) = x^2+1$, $h(x)=2x-5$ where $f : \mathbb{R} \rightarrow \mathbb{R}$, $g: \mathbb{R} \rightarrow \mathbb{R}$, $h : \mathbb{R} \rightarrow \mathbb{R}$ find $f \circ g$, $g \circ h$, $f \circ h$ 6
- (c) Find all possible laurent's series for $f(z) = \frac{4z+3}{z(z-3)(z+2)}$ indicating the region of convergence. 8
5. (a) Let G be the set of rational numbers different from 1. Let $a*b = a+b-ab$ for all $a, b \in G$. Prove that $(G, *)$ is a group. 6
- (b) The number of car accidents in a metropolitan city was found to be 20, 17, 12, 6, 7, 15, 8, 5, 16, 14 per month respectively. Use χ^2 - test to check whether these frequencies are in agreement with the belief that occurrence of accidents was the same during 10 months period. 6
- (c) Check whether $A = \{2, 4, 12, 16\}$ and $B = \{3, 4, 12, 24\}$ are lattices under divisibility. Draw their Hasse diagrams. 8
6. (a) Use Cayley-Humilton theorem to find 6
- $$2A^5 - 3A^4 + A^2 - 5I \text{ where } A = \begin{bmatrix} 3 & 1 \\ -1 & 2 \end{bmatrix}$$
- (b) Fit a Bionomial distribution to the following data 6
- | | | | | | | | |
|-----|-----|----|----|----|---|---|---|
| x | : 0 | 1 | 2 | 3 | 4 | 5 | 6 |
| f | : 5 | 18 | 28 | 12 | 7 | 6 | 4 |
- Also calculate the expected frequencies.
- (c) Find the characteristic equation of the matrix A and verify that it is satisfied by 8
- $$A \text{ and hence find } A^{-1} \text{ where } A = \begin{bmatrix} 2 & -1 & 1 \\ -1 & 2 & -1 \\ 1 & -1 & 2 \end{bmatrix}$$
7. (a) Ten individuals are chosen at random from a population and their heights are found to be 63, 63, 64, 65, 66, 69, 69, 70, 70, 71 inches. discuss the suggestion that the mean height of the universe is 65 inches. 6
- (b) An insurance company found that only 0.01% of the population is involved in a certain type of accident each year. If its 1000 policy holders were randomly selected from the population, what is the probability that not more than two of its clients are involved in such accident next year? 6
- (c) The first four moments of a distribution about the value 5 are 2, 20, 40 and 50 calculate the values of mean, variance, μ_3 , μ_4 . 8


(OLD COURSE)QP Code : **MV-18834**

(3 Hours)


[Total Marks : 100

N.B. (1) Question no. 1 is compulsory.(2) Attempt any **four** questions out of questions no. 2 to 7.

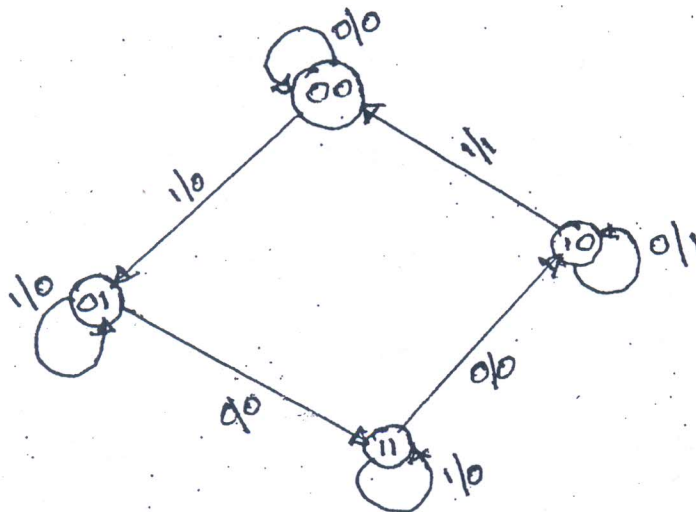1. (a) Explain Moore and Mealy sequential circuits. 5
 (b) List the predefined datatypes and their declarations in VHDL. 5
 (c) Compare synchronous and Asynchronous sequential machines. 5
 (d) Compare SRAM and DRAM memory. 5
2. (a) Write a VHDL code for multiplexer IC 74151. 10
 (b) With reference to XC 9500 CPLD family explain : 10
 - (i) Architecture of functional block
 - (ii) Product term allocator and macro cell architecture.
3. (a) What are ring counters and twisted ring counter. Design Johnson counter using IC 74194 universal shift register. 10
 (b) For the state diagram shown below design the clocked sequential circuit using T flipflops. 10



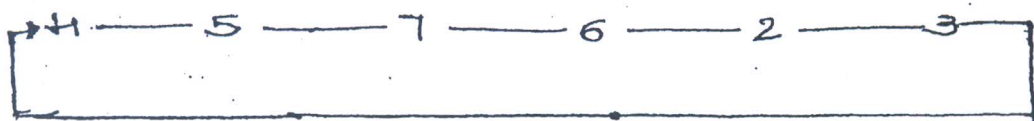4. (a) Design asynchronous counter using JK flipflops which runs through a sequence of 10



Flipflop responds to a positive edge of a clock pulse.


- (b) Using structural modeling, write a VHDL code for full adder by using half adder. 10

[TURN OVER

5. (a) Reduce the state table using implication chart method and design state machine using DFF. Use decoder for generation of excitation inputs. 10

Present State	Next state			
	x=0	z	x=1	z
S ₀	S ₄	0	S ₃	1
S ₁	S ₅	0	S ₃	0
S ₂	S ₄	0	S ₁	1
S ₃	S ₅	0	S ₁	0
S ₄	S ₂	0	S ₅	1
S ₅	S ₁	0	S ₂	0

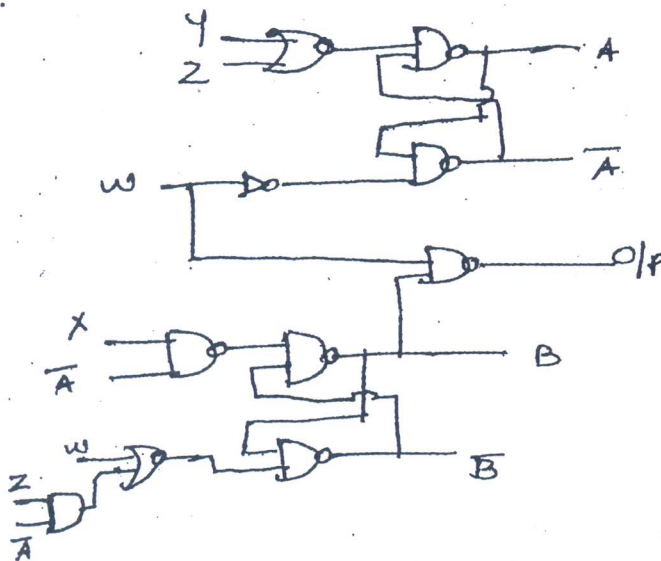- (b) Write a VHDL code for mod 8 synchronous counter. 10
6. (a) Design a mod-8 synchronous counter using JK flipflop. Also draw a timing diagram. 10
- (b) Write notes on : - 10
- (i) Different modeling styles in VHDL
 - (ii) Application of shift registers
7. (a) Analyse the pulse mode asynchronous sequential machine and obtain the state diagram. 10



- (b) Draw and explain SRAM architecture. 10

ECAD

(OLD COURSE)

QP Code No. MV-18873

(3 Hours)

[Total Marks : 100]

- N.B. (1) Question No. one is compulsory.
 (2) Attempt any four questions from remaining six questions.
 (3) Assume suitable data if necessary
 (4) Figures to right indicate full marks.

1. Solve any four from the following :-

20

- Compare a.c. small signal amplifiers using BJT and using JFET. Consider input resistance, voltage gain and maximum output voltage swing.
- Differentiate between a.c. small signal amplifiers and a.c. large signal amplifiers.
- Compare CE and CB amplifiers considering thermal stability S_{ICO}
- Explain why constant current sources are used in differential amplifiers.
- Give important features of CASCODE amplifier.

2. Design a two stage R-C coupled amplifier for the following specifications :-

20

$$A_v > 850, \quad S_{ICO} < 8, \quad R_1 = 5 \text{ K}\Omega$$

$$V_{CC} = 24\text{V}, \quad f_L < 15 \text{ Hz.}$$


Select appropriate transistors from the data table given at the end of question paper.

Neglect h_{re} and h_{oe}

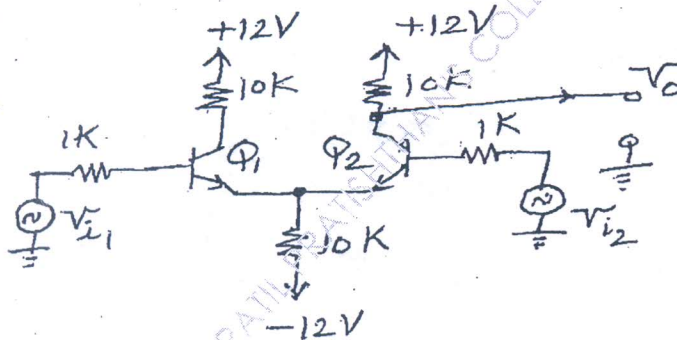3. For differential amplifier shown in figure below determine-

20


- Q points of transistors
- Differential voltage gain (A_d)
- Common mode voltage gain (A_c).



Transistors Q_1 and Q_2 are BC 147 A
 (refer to data table for transistor data)
 Neglect h_{oe} & h_{re}



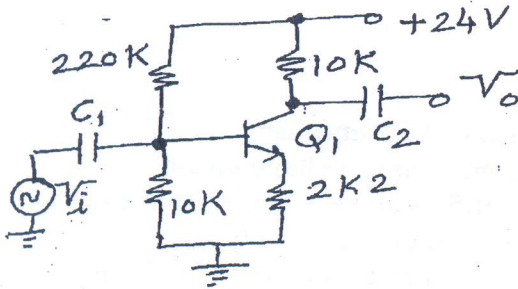4. (a) For amplifier circuit shown in figure below using negative feedback approach determine type of feedback, stability ratio, A_{v_f} and A_{i_f} 15



$$h_{ie} = 1k\Omega$$

$$h_{fe} = 80$$

(Neglect h_{re} and h_{oc})

- (b) Explain the difference between a.c. small signal amplifier and power amplifier. 5
5. (a) Design class B power amplifier using transformer coupling to obtain 5 Watt output in 4 ohm load. Assume V_{CC} 12V and select suitable transistors from the data table. 15
- (b) Differentiate between class A, class B and class C amplifiers. 5
6. (a) Draw circuit diagram of R-C phase shift oscillator. Design the circuit for oscillation frequency of 2 kHz. Assume d.c. supply of 12 V and select suitable transistor from the data table. Neglect h_{re} and h_{oc} . 15
- (b) Explain how stability of amplifier with feedback is determined. 5
7. Write short notes on any three of the following :- 20
- Nyquist plot
 - Colpitts oscillator
 - Cross over distortion in class B amplifier.
 - Crystal oscillator.



[TURN OVER

DBEC DATA SHEET

Transistor type	P _{dm} max @ 25°C Watts	I _{cm} max @ 25°C Amps	V _{CE(sat)} volts d.c.	V _{CE0} volts d.c.	V _{CE0} (Sust) volts d.c.	V _{CE(sat)} volts d.c.	V _{CE0} volts d.c.	V _{BE0} volts d.c.	T _j max °C	D.C. current gain		Small Signal		h _{FE} max.	V _{BE} max.	D _{th} °C/W	Derate above 25°C W/°C
										min	typ.	min.	typ.				
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	70	15	50	120	1.8	1.5	0.7
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	100	25	75	125	1.5	3.5	0.4
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	110	33	60	115	1.2	4.0	0.3
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	280	50	90	280	0.9	35	0.05
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	125	220	260	0.9	—	—
2N 525(PNP)	0.225	0.5	0.25	85	50	—	—	—	100	35	65	—	45	—	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	450	240	330	500	0.9	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

Transistor type	h _{ie}	h _{oe}	θ _{ja}	-V _{GS} volts		I _{DS} max. mA		I _{DS} typ. mA		I _{DS} min. mA		-V _{GS} Volts		r _d	Derate above 25°C	θ _{ja}
				0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4			
BC 147A	2.7 K Ω	18 μ Ω	1.5 × 10 ⁻⁴	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0	4.0
2N 525 (PNP)	1.4 K Ω	25 μ Ω	3.2 × 10 ⁻⁴	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0	0.0
BC 147B	4.5 K Ω	30 μ Ω	2 × 10 ⁻⁴	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0	0.0
ECN 100	50 Ω	—	—	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0
ECN 149	15 Ω	—	—	—	—	—	—	—	—	—	—	—	—	—	—	—
ECN 055	12 Ω	—	—	—	—	—	—	—	—	—	—	—	—	—	—	—
2N 3055	6 Ω	—	—	—	—	—	—	—	—	—	—	—	—	—	—	—

N-Channel JFET

Type	V _{DS} max. Volts	V _{GS} max. Volts	P _d max. @ 25°C	T _j max.	I _{DSS}	-V _{GS} Volts	r _d	Derate above 25°C	θ _{ja}
2N3822	50	50	300 mW	175°C	2 mA	6	50 KΩ	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	300 mW	200°C	7 mA	2.5	50 KΩ	—	0.59°C/mW





BADCS.

(OLD COURSE)**QP Code : MV-18910**

(3 Hours)

[Total Marks : 100

- N.B.** (1) Assume suitable data if any.
 (2) Question No. 1 is **compulsory**.
 (3) Solve any **four** questions from **remaining**.

- | | |
|--|----|
| 1. (a) Explain elements of communication. | 20 |
| (b) What is need of modulation ? | |
| (c) Explain VSB system. | |
| (d) Explain function of R.F. Amplifier in radio receiver stage | |
| (e) Explain Sampling theorem. | |
| 2. (a) Explain function of Balance modulator in A.M. | 10 |
| (b) Explain ISB system. | 10 |
| 3. (a) Explain indirect F.M. generation technique. | 10 |
| (b) Draw any explain frequency spectrum of F.M. system. | 5 |
| (c) Compare narrow band and wide band of F.M. | 5 |
| 4. (a) What is need of Superhetrodyne Radio Receiver ? | 10 |
| (b) Explain ratio detector. | 10 |
| 5. (a) Explain PCM system. | 10 |
| (b) What is aliasing effect, how to avoid it ? | 10 |
| 6. (a) Explain PWM system. | 10 |
| (b) Explain Adaptive Delta modulator. | 10 |
| 7. Write short notes on any three :— | 20 |
| (a) FDM | |
| (b) Modulation index of AM | |
| (c) Delta modulator | |
| (d) Filter method for SSB generation. | |

Con. 13425-14.